

---

# 10ES32 - Analog Electronic Circuits

## Assignment-II

- Note:
- i) Write the assignment in a A4 size paper
  - ii) Mention your USN, name and section on the top right corner of first page
  - iii) Assume the missing data suitably
  - iv) Submit the assignment on or before 11.00 AM, Monday, 7/10/2013
- 

1. Explain transistor switching network.
2. Derive the expressions for  $S$ ,  $S'$ , and  $S''$  for i) Emitter Bias, ii) Voltage Divider Bias, and iii) Collector Feedback Bias.
3. Design a voltage divider bias circuit to get the Q point  $I_{CQ} = 3\text{mA}$  and  $V_{CEQ} = 7\text{V}$ .
4. Design a emitter bias circuit to get the Q point  $I_{CQ} = 2.1\text{mA}$  and  $V_{CEQ} = 5\text{V}$ .
5. Design a collector feedback bias circuit to get the Q point  $I_{CQ} = 1\text{mA}$  and  $V_{CEQ} = 6\text{V}$ .
6. For a voltage divider bias circuit,  $R_1 = 62\text{ K}\Omega$ ,  $R_2 = 9.1\text{ K}\Omega$ ,  $R_E = 680\ \Omega$ ,  $R_C = 3.9\text{ K}\Omega$ ,  $V_{CC} = 16\text{V}$ ,  $\beta = 80$ , calculate  $S$  and  $S'$ .
7. Determine the stability factor  $S(\beta)$  and the change in  $I_C$  from  $25^\circ\text{C}$  to  $100^\circ\text{C}$  for the transistor with  $\beta(25^\circ\text{C}) = 50$  and  $\beta(100^\circ\text{C}) = 100$  for the following bias arrangement.
  - a) Fixed bias with  $R_B = 330\text{ K}\Omega$
  - b) Emitter bias with  $R_B/R_E = 5$
  - c) Voltage divider bias with  $R_{TH}/R_E = 1.5$Also calculate  $I_{CQ}$  at the  $100^\circ\text{C}$  in each case if  $I_{CQ}$  at  $25^\circ\text{C}$  is  $3\text{ mA}$
8. What is Barkhausen criterion? Explain how oscillations start in an oscillator.
9. Design a transistor Hartley oscillator to generate a frequency of  $175\text{KHz}$ . Consider  $H_{fe} = 45$ .
10. Explain the merits and demerits of RC phase shift oscillator
11. A quartz crystal has  $L = 0.12\text{H}$ ,  $C = 0.04\text{ pF}$ ,  $C_M = 1\text{pF}$  and  $R = 9.2\text{ k}\Omega$ . Find i) Series resonant frequency, ii) Parallel resonant frequency and iii) Quality factor.